



$$A_V = \frac{V_2}{V_1}$$

$$i_b = \frac{V_1}{R_{BE}}$$

$$i_c = \beta \cdot i_b$$

$$i_e = i_b + i_c = i_b(\beta + 1)$$

$$V_{BE} = V_1 - V_2$$

$$V_2 = i_e \cdot R_E = R_E \cdot i_b(\beta + 1) = R_E \cdot (i_b \cdot \beta + i_b) = R_E \left( \frac{V_2}{R_{BE}} + \frac{\beta V_{BE}}{R_{BE}} \right)$$

$$= R_E \cdot V_{BE} \left( \frac{1}{R_{BE}} + \frac{\beta}{R_{BE}} \right)$$

$$\text{krav 1 } \beta \gg 1 \Rightarrow \frac{\beta}{R_{BE}} \gg \frac{1}{R_{BE}}$$

$$\Rightarrow R_E \cdot V_{BE} \cdot \frac{\beta}{R_{BE}}$$

$$V_2 = (V_1 - V_2) R_E \cdot \frac{\beta}{R_{BE}} \Rightarrow A_V = \frac{V_2}{V_1} = \frac{\frac{R_E \beta}{R_{BE}} \cdot \frac{R_{BE}}{\beta}}{1 + \frac{R_E \beta}{R_{BE}} \cdot \frac{R_{BE}}{\beta}}$$

$$A_V = \frac{R_E}{\frac{R_{BE}}{\beta} + R_E}$$

$$\text{krav 2 } \frac{R_{BE}}{\beta} \ll R_E$$

$$A_V \approx \frac{R_E}{R_E}$$

$$\approx 1$$

$$\text{krav 1: } \beta \gg 1$$

$\beta$  er vanligvis i størrelsesorden  $10^2$  eller større

$$\text{krav 2: } \frac{R_{BE}}{\beta} \ll R_E$$

$\frac{R_{BE}}{\beta}$  er vanligvis i størrelsesorden  $10^1$  eller mindre, mens  $R_E$  er

i størrelsesorden  $10^2$  eller høyere

Håken K. Mikalsen